

Terminology

Literal

- Each appearance of a variable, either uncomplemented or complemented, in a logical term is called a *literal*.
- For example
 - Product term $x_1x_2x_3$ has three literals
 - Sum term $(x_1' + x_3 + x_4' + x_6)$ has four literals.

Implicant

A product term that indicates the input valuation(s) for which a given function is equal to 1 is called an *implicant* of the function. The most basic implicants are the minterms.

Prime Implicant

An implicant is called a *prime implicant* if it cannot be combined into another implicant that has fewer literals.

Example:

$$f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7).$$

- There are 11 implicants for this function:
 - **five minterms:** $x_1'x_2'x_3'$, $x_1'x_2'x_3$, $x_1'x_2x_3'$, $x_1'x_2x_3$, and $x_1x_2x_3$.
 - **five implicants** that correspond to all possible pairs of minterms: $x_1'x_2'$ (m0 and m1), $x_1'x_3'$ (m0 and m2), $x_1'x_3$ (m1 and m3), $x_1'x_2$ (m2 and m3), and x_2x_3 (m3 and m7).
 - **one implicant** that covers a group of four minterms: x_1' .
- Here there are two prime implicants: x_1' and x_2x_3 .

x_1x_2	00	01	11	10
x_3				
0	1	1	0	0
1	1	1	1	0

x_1x_2	00	01	11	10
x_3				
0	1	1	0	0
1	1	1	1	0


\bar{x}_1 (grouping the first column, minterms 0, 1, 2, 3)

x_2x_3 (grouping the minterms 3 and 7)

$$f = \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1x_2x_3 + x_1x_2x_3$$

$$f = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_2x_3$$

$$f = \bar{x}_1 + x_2x_3$$

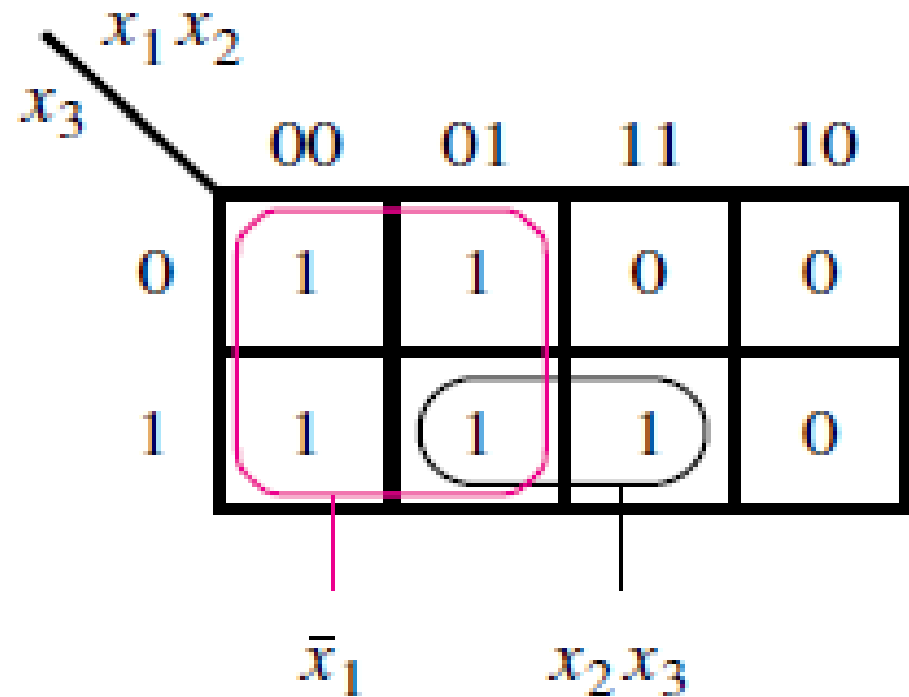

While all of these expressions represent the function f correctly, the cover consisting of prime implicants leads to the lowest-cost implementation.

Cost

- Cost of a logic circuit is the number of gates plus the total number of inputs to all gates in the circuit.
- If we assume that the input variables are available in both true and complemented forms, then the cost of the expression,

$$f = x_1\bar{x}_2 + x_3\bar{x}_4$$

is 9. Otherwise its cost is 13.

Minimization Procedure

The process of finding a minimum-cost circuit involves the following steps:

1. Generate all prime implicants for the given function f .
2. Find the set of essential prime implicants.
3. If the set of essential prime implicants covers all valuations for which $f = 1$,

Then this set is the desired cover of f

Else

Determine the nonessential prime implicants that should be added to form a complete minimum-cost cover.

Minimization Procedure

Consider the following example:

		X1, x2			
		00	01	11	10
X3, x4	00	0	0	0	0
	01	0	1	1	0
	11	1	1	0	1
	10	1	1	1	1

Here there is a choice as to which prime implicants to include in the final cover


Minimization Procedure

- There are five prime implicants: $x_1'x_3$, $x_2'x_3$, x_3x_4' , $x_2x_3'x_4$, $x_1'x_2x_4$.
- The essential ones are $x_2'x_3$, (because of m_{11}), x_3x_4' (because of m_{14}), $x_2x_3'x_4$ (because of m_{13}).
- They must be included in the cover. These three prime implicants cover all minterms for which $f = 1$ except m_7 . It is clear that m_7 can be covered by either $x_1'x_3$ or $x_1'x_2x_4$

Because $x_1'x_3$ has a lower cost, it is chosen for the cover.

Therefore, the minimum-cost realization is
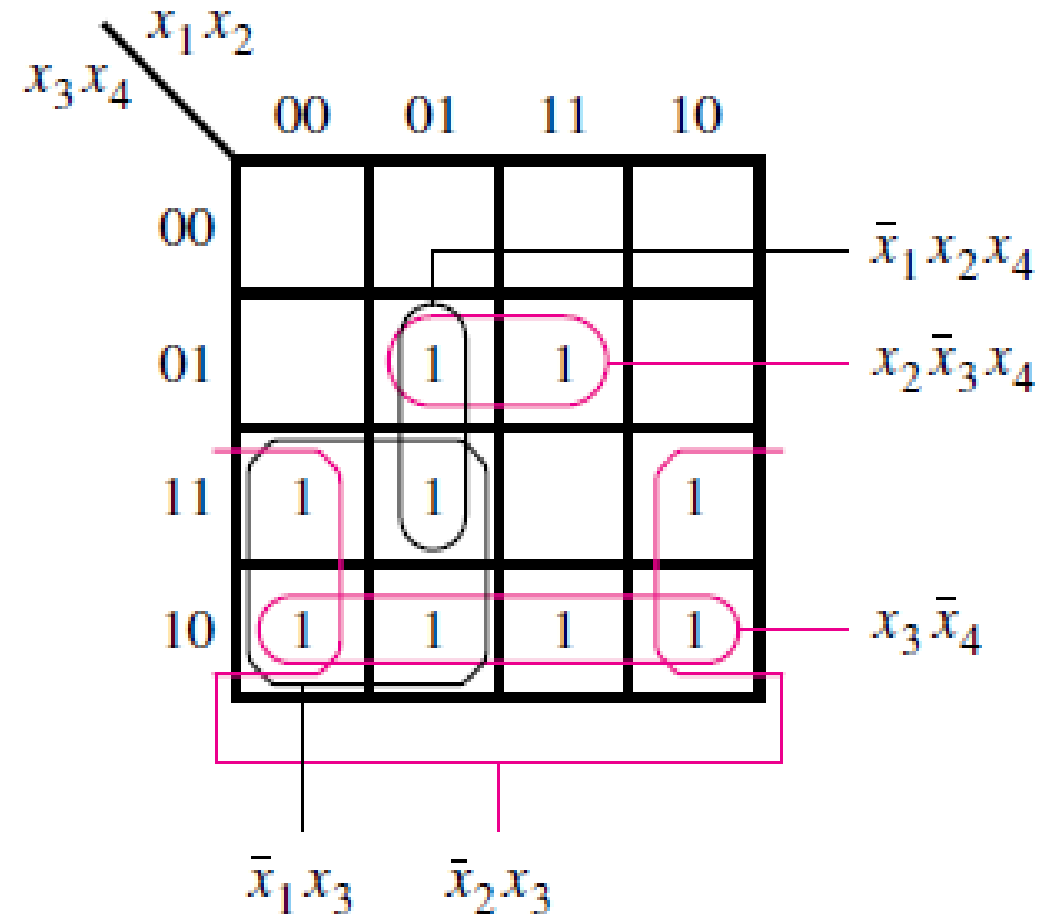
$$f = \bar{x}_2x_3 + x_3\bar{x}_4 + x_2\bar{x}_3x_4 + \bar{x}_1x_3$$



Minimization Procedure

Consider the following example:


		X1, x2			
		00	01	11	10
X3, x4	00	1	1	1	1
	01	0	0	1	0
	11	0	0	1	1
	10	0	0	0	1

Consider the following example:

only $x_3'x_4'$ is essential.

Then the best choice to implement the minimum cost circuit is
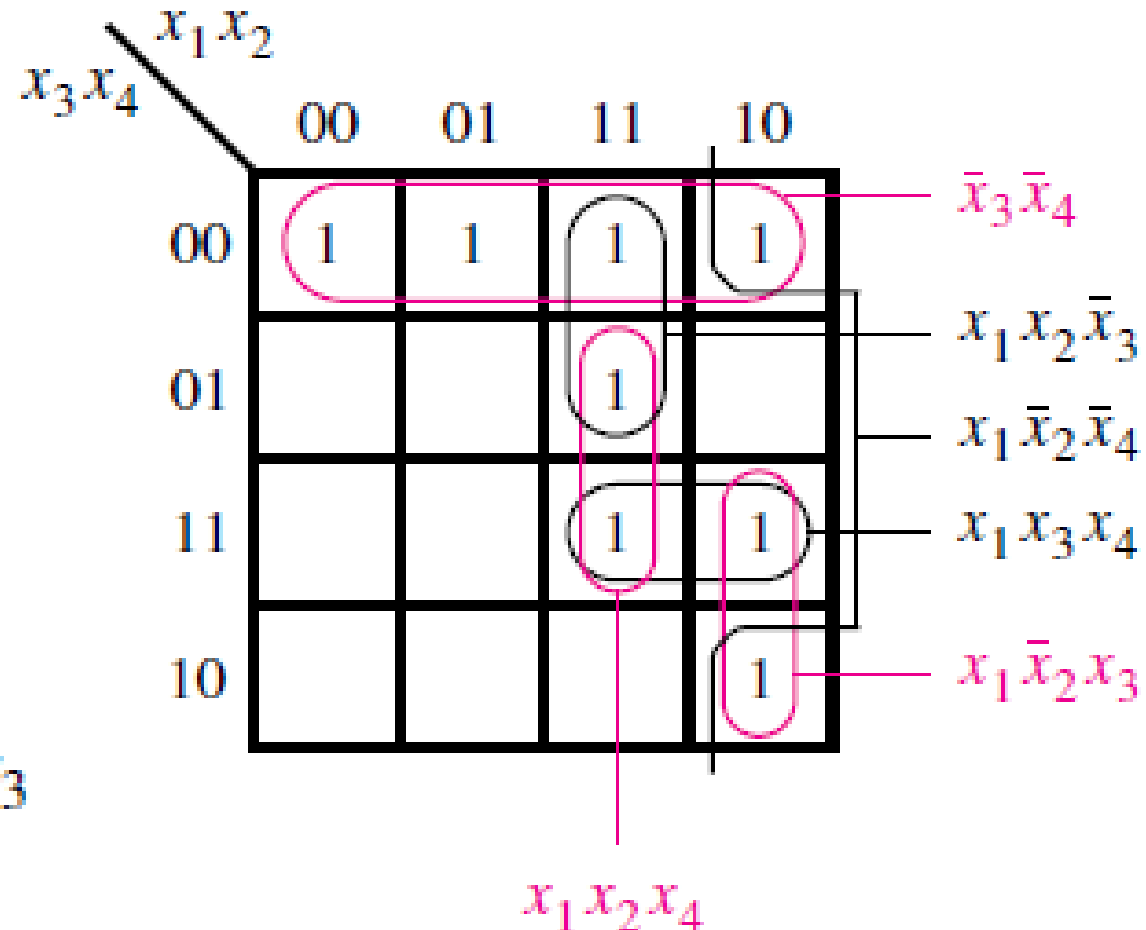
$$f = \bar{x}_3\bar{x}_4 + x_1x_2x_4 + x_1\bar{x}_2x_3$$



Minimization Procedure

Consider the following example:

X3, x4 \ X1, x2	X1, x2			
	00	01	11	10
00	1	1	0	0
01	0	1	1	0
11	0	0	1	1
10	1	0	0	1


There are no essential prime implicants at all.

Sometimes there may not be any essential prime implicants at all.
Example:

Two alternatives:

$$f = \bar{x}_1\bar{x}_3\bar{x}_4 + x_2\bar{x}_3x_4 + x_1x_3x_4 + \bar{x}_2x_3\bar{x}_4$$
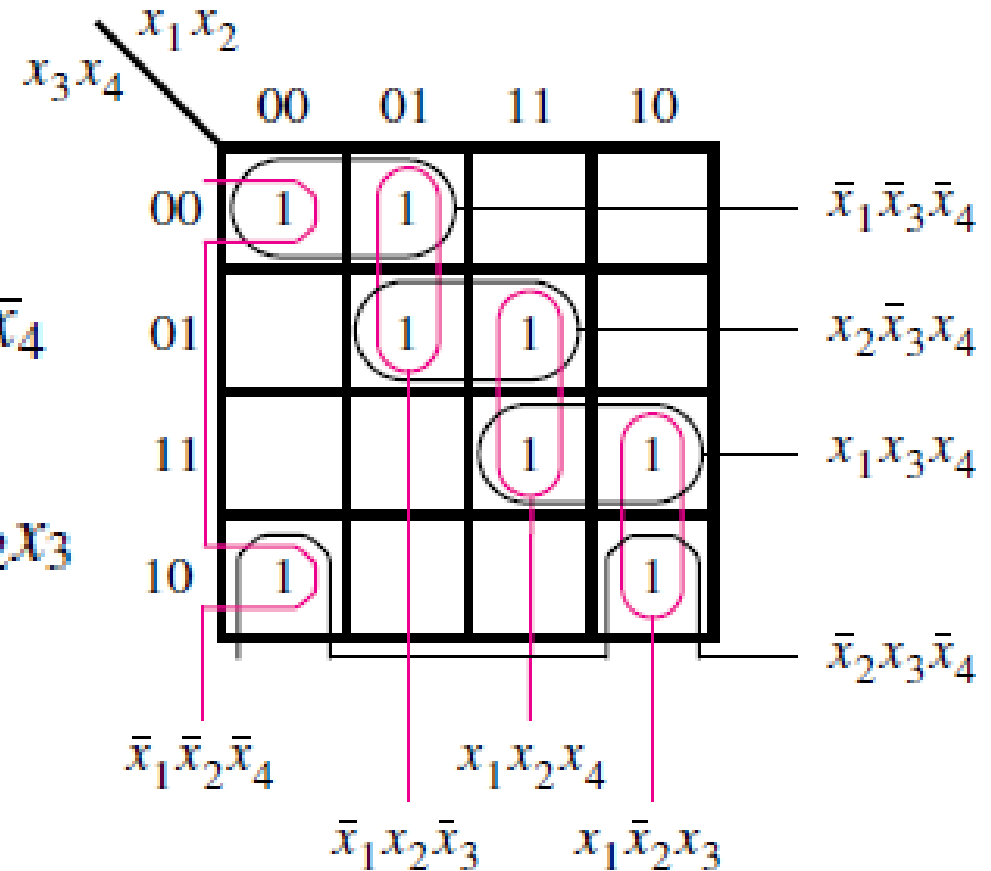
$$f = \bar{x}_1\bar{x}_2\bar{x}_4 + \bar{x}_1x_2\bar{x}_3 + x_1x_2x_4 + x_1\bar{x}_2x_3$$



Minimization of Product-of-Sums Forms


Example1:

x_1x_2		00	01	11	10
x_3					
0	1	1	0	0	
1	1	1	1	0	

Minimization of Product-of-Sums Forms

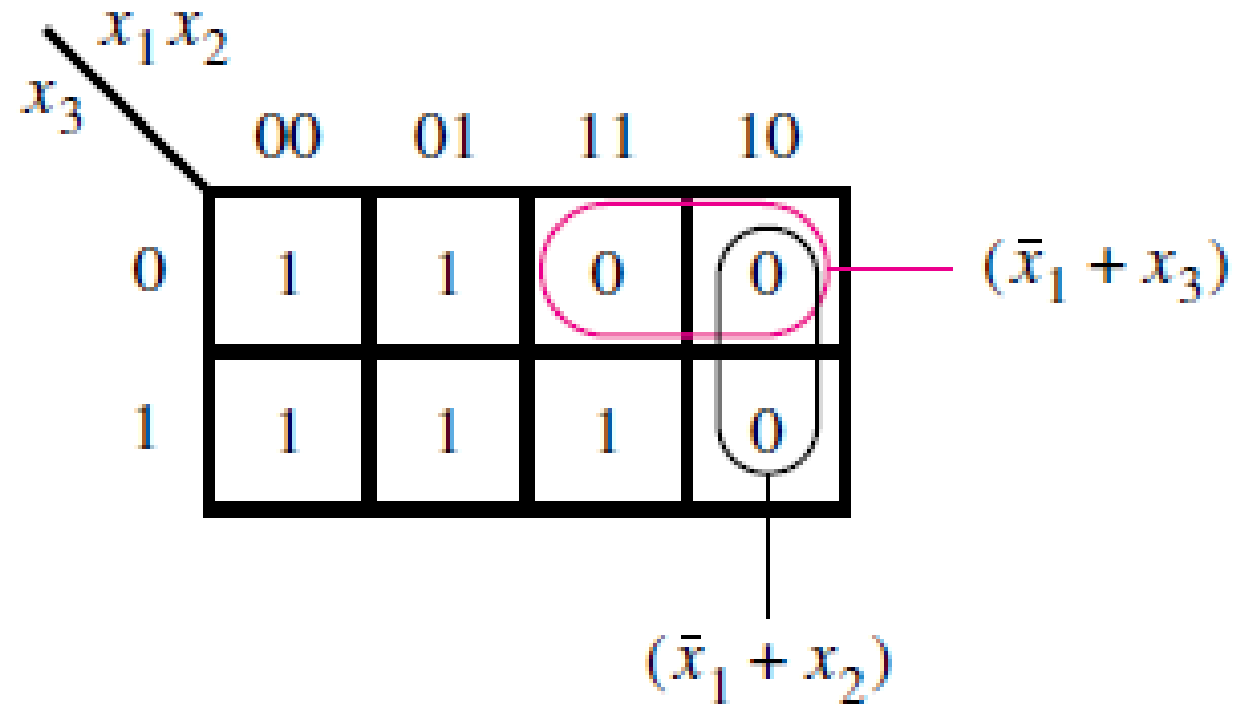Example1:

$$f = (\bar{x}_1 + x_2)(\bar{x}_1 + x_3)$$



Its cost is greater than the cost of the equivalent SOP implementation

$$f = \bar{x}_1 + x_2x_3$$

SOP COST: 6 (assuming input variables are available in both true and complemented forms)

$$f = (\bar{x}_1 + x_2)(\bar{x}_1 + x_3)$$

POS COST: 9

Example2:

X3, x4 \ X1, x2	X1, x2			
	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	1	1	0	1
10	1	1	1	1

Assuming that both the complemented and uncomplemented versions of the input variables x_1 to x_4 are available,

$$f = \bar{x}_2 x_3 + x_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + \bar{x}_1 x_3 \quad \text{SOP} \quad \text{COST: 18}$$

$$f = (x_2 + x_3)(x_3 + x_4)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4) \quad \text{POS COST: 15}$$

SOP and POS implementations of a given function may or may not entail the same cost.

Incompletely Specified Functions

In digital systems it often happens that certain input conditions can never occur. For example, suppose that x_1 and x_2 control two interlocked switches such that both switches cannot be closed at the same time. Then the input valuations $(x_1, x_2) = 11$ is guaranteed not to occur. Then we say that $(x_1, x_2) = 11$ is a don't-care condition, meaning that a circuit with x_1 and x_2 as inputs can be designed by ignoring this condition. A function that has don't-care condition(s) is said to be incompletely specified.

Incompletely Specified Functions

- A function that has don't-care condition(s) is said to be incompletely specified.
- The don't cares are denoted by the letter d in the map.
- A function with don't care condition is specified as follows:

$$f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

where D is the set of don't-cares.

$$f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

X3, x4 \ X1, x2	X1, x2			
	00	01	11	10
00	0	1	d	0
01	0	1	d	0
11	0	0	d	0
10	1	1	d	1

Incompletely Specified Functions

$x_1 x_2$		$x_3 x_4$			
		00	01	11	10
$x_3 x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1

$x_2 \bar{x}_3$ (points to the 2x2 group of 1s in the first two columns)
 $x_3 \bar{x}_4$ (points to the 1x4 group of 1s in the bottom row)

(a) SOP implementation

$$f = x_2 \bar{x}_3 + x_3 \bar{x}_4$$

$x_1 x_2$		$x_3 x_4$			
		00	01	11	10
$x_3 x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1

$(x_2 + x_3)$ (points to the 2x2 group of 0s in the first two columns)
 $(\bar{x}_3 + \bar{x}_4)$ (points to the 1x4 group of 0s in the third column)


(b) POS implementation

$$f = (x_2 + x_3)(\bar{x}_3 + \bar{x}_4)$$

Minimal SoP or PoS – two levels

NAND and NOR Implementation

$$f = x_2 + x_1\bar{x}_3$$

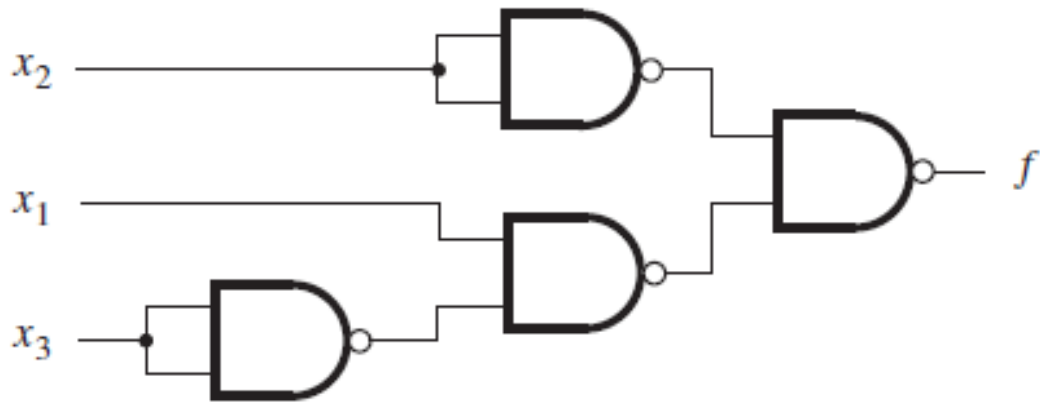

$$f = (x_1 + x_2)(x_2 + \bar{x}_3)$$

