

Using Verilog Constructs for Storage Elements

```
module flipflop (D, Clock, Q);  
input D, Clock;  
output reg Q;  
always @(posedge Clock)  
    Q = D;  
endmodule
```

```
`timescale 1ns/1ps
```

```
module flipflop_tb();
```

```
    reg D, Clock;
```

```
    wire Q;
```

```
    // Instantiate the DUT (Device Under Test)
```

```
    flipflop uut (
```

```
        .D(D),
```

```
        .Clock(Clock),
```

```
        .Q(Q)
```

```
    );
```

```
// Clock generation: Toggle every 5ns → 10ns period (100MHz)
```

```
initial begin
```

```
    Clock = 0;
```

```
    forever #5 Clock = ~Clock;
```

```
end
```

```
// Apply stimulus
```


```
initial begin
```

```
    // Monitor signals
```

```
    $monitor("Time=%0t | D=%b | Clock=%b | Q=%b", $time, D,  
Clock, Q);
```


```
// Initial values
```

```
    D = 0;
```

 

```
module example5_3 (D, Clock, Q1, Q2);
input D, Clock;
output reg Q1, Q2;
always @(posedge Clock)
begin
  Q1 = D;
  Q2 = Q1;
end
endmodule
```

 Incorrect code for two cascaded flip-flops



```
module example5_4 (D, Clock,
Q1, Q2);
input D, Clock;
output reg Q1, Q2;
always @(posedge Clock)
begin
  Q1 <= D;
  Q2 <= Q1;
end
endmodule
```

Blocking and Non-Blocking Assignments

$f = x1 \& x2;$

This notation is called a *blocking* assignment.

A Verilog compiler evaluates the statements in an **always** block in the order in which they are written.


If a variable is given a value by a blocking assignment statement, then this **new value is used in evaluating all subsequent statements in the block.**

Verilog also provides a *non-blocking* assignment, denoted with `<=`.

All non-blocking assignment statements in an **always** block are evaluated using the values that the variables have when the **always** block is entered.

Thus, a given variable has the same value for all statements in the block.

 
The meaning of non-blocking is that the result of each assignment is not seen until the end of the **always** block.



```

module example5_5 (x1, x2, x3,
Clock, f, g);
input x1, x2, x3, Clock;
output reg f, g;
always @(posedge Clock)
begin
  f = x1 & x2;
  g = f | x3;
end
endmodule

```

 

```

module example5_6 (x1, x2, x3, Clock, f, g);
input x1, x2, x3, Clock;
output reg f, g;
always @(posedge Clock)
begin
  f <= x1 & x2;
  g <= f | x3;
end
endmodule

```



ASYNCHRONOUS CLEAR

Following module defines a D flip-flop with an asynchronous active-low reset (clear) input.

When *Resetn*, the reset input, is equal to 0, the flip-flop's Q output is set to 0.

The sensitivity list specifies the negative edge of *Resetn* as an event trigger along with the positive edge of the clock.

We cannot omit the keyword **negedge** because the sensitivity list cannot have both edge-triggered and level sensitive signals.


```

module flipflop (D, Clock, Q);
input D, Clock;
output reg Q;
always @(posedge Clock)
Q <= D;
endmodule

```

DFF with no reset

```

module flipflop (D, Clock, Resetn, Q);
input D, Clock, Resetn;
output reg Q;
always @(negedge Resetn or posedge Clock)
if (!Resetn)
Q <= 0;
else
Q <= D;
endmodule

```

DFF with asynchronous active low reset

```

module flipflop (D, Clock, Resetn, Q);
input D, Clock, Resetn;
output reg Q;
always @(posedge Clock)
if (!Resetn)
Q <= 0;
else
Q <= D;
endmodule

```

DFF with synchronous active low reset

D flip-flop with asynchronous active-low reset.

Key points: Reset is asynchronous. Because the always block is sensitive to negedge Resetn.

As soon as Resetn goes low, output Q is immediately forced to 0 (even without waiting for clock). Clock is positive-edge triggered.

On every rising edge of clock, if reset is not active, Q takes the value of D.

This is called D flip-flop with asynchronous active-low reset.

Code for an n -bit register with asynchronous clear

```
module regn (D, Clock, Resetn, Q);  
parameter n = 16;  
input [n-1:0] D;  
input Clock, Resetn;  
output reg [n-1:0] Q;  
always @(negedge Resetn, posedge Clock)  
if (!Resetn)  
    Q <= 0;  
else  
    Q <= D;  
endmodule
```

Code for an n -bit register with asynchronous clear

This is an n -bit register with asynchronous active-low reset: If reset is active ($\text{Reset}_n=0$) \rightarrow output Q becomes 0 immediately. On each rising edge of the clock, if reset is not active, Q takes the value of input D .

👉 Essentially, it's a D flip-flop register with parameterized width and asynchronous reset.

Code for a four-bit shift register(right shift)

```
module shift4 (w, Clock, Q);  
input w, Clock;  
output reg [3:0] Q;  
always @(posedge Clock)  
begin  
    Q[0] <= Q[1];  
    Q[1] <= Q[2];  
    Q[2] <= Q[3];  
    Q[3] <= w;  
end  
endmodule
```

```
for (k = 0; k < n - 1; k = k + 1)  
    Q[k] <= Q[k + 1];  
Q[n - 1] <= w;
```

$w \rightarrow$ a 1-bit serial input.

Clock \rightarrow the clock signal.

Q is declared as a **4-bit register** (Q[3:0]) that stores the shifted data.
always @(posedge Clock)

This block runs on every rising edge of the clock.

The shifting operation is synchronous with the clock.

The values are updated as follows:

Q[0] takes the previous value of Q[1]. Q[1] takes the previous value of Q[2]. Q[2] takes the previous value of Q[3]. Q[3] takes the new serial input w

This makes it a 4-bit Serial-In / Parallel-Out (SIPO) shift register.

```
module ring_count(q,clk,clr);  
input clk,clr;  
output [3:0]q;  
reg [3:0]q;  
always @(posedge clk)  
if(clr==1)  
q<=4'b1000;  
else  
begin  
q[3]<=q[0];  
q[2]<=q[3];  
q[1]<=q[2];  
q[0]<=q[1];  
end  
endmodule
```

Lab - 7

1. Write behavioral Verilog code for a negative edge triggered T FF with asynchronous active low reset.
2. Write behavioral Verilog code for a positive edge-triggered JK FF with synchronous active high reset
3. Design and simulate the following counters
 - a) 4-bit ring counter.
 - b) 5 bit Johnson counter.

Code for negative edge triggered T FF with asynchronous active low reset

```
module tff(T,Clk,Q,Reset);  
input T,Reset,Clk;  
output Q;  
reg Q;  
always@(negedge Clk or negedge Reset)  
if(!Reset)  
Q<=0;  
else if(T==1)  
Q<=~Q;  
endmodule
```

Code for positive edge triggered JK FF with synchronous active high reset

```
module jkff(J,K,Clk,Reset,Q);
input J,K,Clk,Reset;
output Q;
reg Q;
always@(posedge Clk)
if(Reset)
Q<=0;
else
begin
case({J,K})
2'b00:Q<=Q;
2'b01:Q<=0;
2'b10:Q<=1;
2'b11:Q<=~Q;
endcase
end
endmodule
```

Ring Counter 2-bit counter and 2to4 decoder

```
module ring (clk,q);
input clk;
output [3:0]q;
wire [1:0] count;
bitcounter2 one(clk,count[1:0]);
d2to4 two(en, count[1:0],q[3:0]);
endmodule

module dff11(clk,d,q);
input clk,d;
output q;
reg q;
always@(posedge clk)
begin
q<=d;
end
endmodule
```

```
module d2to4(en,w,y);
input en;
input [1:0]w;
output [3:0]y;
reg [3:0]y;
always@(en or w)
begin
y=0;
if(en==1)
case(w)
0:y[3]=1;
1:y[2]=1;
2:y[1]=1;
3:y[0]=1;
endcase
end
endmodule
```

```
module bitcounter2(clk,q);
input clk;
output[1:0]q;
dff11 ffo(clk,q[1]^q[0],q[1]);
dff11 ff1(clk,~q[0],q[0]);
endmodule
```

Johnson Counter

```
module johnson(clk,q);  
input clk;  
output [4:0]q;  
dff1 ffo(clk,~q[4],q[0]);  
dff1 ff1(clk,q[0],q[1]);  
dff1 ff2(clk,q[1],q[2]);  
dff1 ff3(clk,q[2],q[3]);  
dff1 ff4(clk,q[3],q[4]);  
endmodule
```

```
module dff1(clk,d,q);  
input clk,d;  
output q;  
reg q;  
always@(posedge clk)  
begin  
q=d;  
end  
endmodule
```

1. Write behavioral Verilog code for a negative edge triggered T FF with asynchronous active low reset.


```
module l6q2(t, clock, reset,q);  
input t, clock,reset;  
output q;  
reg q;  
always@ (negedge clock or negedge reset)  
begin  
if(!reset)  
q<=0;  
else  
case(t)  
0:q<=q;  
1:q<=~q;  
endcase  
end  
endmodule
```

2. Write behavioral Verilog code for a positive edge-triggered JK FF with synchronous active high reset.

```
module l6q1(j,k,clock,reset,q);  
input j,k,clock,reset;  
output q;  
reg q;  
always@ (posedge clock)  
begin  
if(reset)  
q<=0;  
else  
case({j,k})  
0:q<=q;  
1:q<=0;  
2:q<=1;  
3:q<=~q;  
endcase  
end  
endmodule
```

Lab 7
1. 4 bit up counter

```
module sync_4bitup(m, clk, En);  
    input En;  
    input clk;  
    output [3:0]m;  
    tfflipflop stage1(En, clk, m[0]);  
    tfflipflop stage2(En & m[0], clk, m[1]);  
    tfflipflop stage3(En & m[1]& m[0], clk, m[2]);  
    tfflipflop stage4(En & m[2]& m[1]& m[0], clk, m[3]);  
endmodule  
  
module tfflipflop(T, clock, Q);  
    input T, clock;  
    output Q;  
    reg Q;  
    always@ (posedge clock)  
    if(T)  
        Q <= ~Q;  
endmodule
```

 



Lab 7 (done similar with x=0 up and x=1 down in class

2. 3 bit up/down counter

UD = 1, up

UD =0, down

 

```
module sync_3bitupdown(clk,UD,Q);
```

```
input UD;
```

```
input clk;
```

```
output [2:0]Q;
```

```
wire control;
```

```
  tflipflop stage1(1, clk, Q[0]);
```

```
  tflipflop stage2((UD & Q[0])|(~UD & ~Q[0]), clk, Q[1]);
```

```
  tflipflop stage3((UD & Q[0] & Q[1])|(~UD & ~Q[0] & ~Q[1]), clk, Q[2]);
```

```
endmodule
```

```
module tflipflop(T, clock, Q);
```

```
input T, clock;
```

```
output Q;
```

```
reg Q;
```

```
always@ (posedge clock)
```

```
if(T)
```

```
  Q <= ~Q;
```

```
endmodule
```